

Low Power SRAM

August Bresnaider

ECE 4332

University of Virginia

etc3xg@virginia.edu

ABSTRACT

Having designed 1Mb of low-power SRAM, this document highlights some of the crucial design decisions that came into play, as well as an analysis of critical metrics, including delay, active/idle power, and total area. Lastly, the robustness of the architecture is supported by verification of its viability within large ranges of process, voltage, and temperature variation.

1. INTRODUCTION

While Moore's Law continues to chug along unimpeded, the modern VLSI industry has not been able to support such advancements to their full potential. It is true that smaller technologies can support lower capacitances and higher frequencies, however, it is also true that power issues like leakage current and efficient heat dissipation have acted as large barriers, hindering all of society's processing power. As such, it becomes increasingly important to address such issues. As researchers, we have developed a proof-of-concept SRAM model using Cadence Virtuoso of 1Mb worth of SRAM. To target low power, we have worked to minimize the following metric:

$$(Active\ Energy\ per\ Access)^2 * Delay * Area * Idle\ Power$$

We decided to use NC State's FreePDK 45nm technology for this model. While we were unable to make changes to the MOSFET layout, we were able to change the gate dimensions and threshold voltages to fit our needs.

1.1 Specifications

To meet specification, our model met the following criteria:

Table 1. Specifications for SRAM Array

Description	Value
Word Size	32b
Inputs	Addr <14:0>, Read, Write, Clock, Din <31:0>
Outputs	Dout <31:0>
Total Model Size	1Mb

The following section details our design decisions of individual parts of the model.

ARCHITECTURE

1.2 Bitcell

Being that our bitcell is the heart and soul of our SRAM's operation, we spent a great deal of time thinking about the sizing of the different transistor types. The bitcell is a prime example of what is called a "ratioed" circuit, in that the gate widths of the technology included within require a certain ratio to operate

correctly. For example: while a large access transistor width may seem desirable in that it would greatly reduce resistance and let the bitline affect the Q value of the cell easier, too large an access transistor can lead to unwieldy amounts of capacitance on the bitlines, slowing down the block's operation dramatically. In our final iteration, we decided on the values as presented in Table 2. In previous iterations, we had settled on much larger access and pull-down transistors, mainly as a fault of our simulations.

Table 2. Bitcell Transistor Gate Dimensions

	Access	Pull-Up	Pull-Down
Width(nm)	150	90	150
Length(nm)	50	50	50

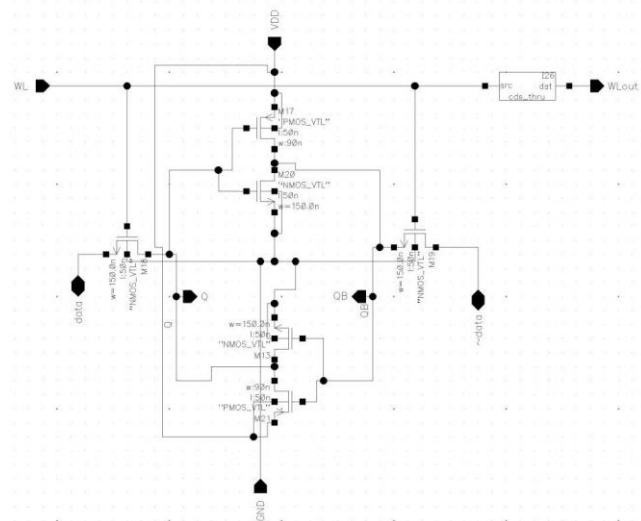



Figure 3. Bitcell Virtuoso Schematic

1.3 Sense Amplifier

To properly output the values stored in our bitcells, we needed a mechanism that would be able to sense differences in bitline voltages and output a value accordingly. While in theory this could be as simple as an inverter, in practice, something of the sort is much too weak and unpredictable, due to near-constant fluctuations in the bitlines, to produce a meaningful output. Instead, we decided on implementing a strong-arm sense amplifier, on account of its functionality as a differential amplifier, as well as its strength in producing a rail-to-rail output[1]. Our implementation can be seen in below:

From these simulations, it was decided that a block would be built of 512 bits per row, and 64 bits per column. The below figure shows a simplified schematic of said block, though due to limitations in simulation, we were unable to include all cells in the schematic, requiring us to make equivalent RC pi models to behave as cells.


Figure 6. Full Block Schematic

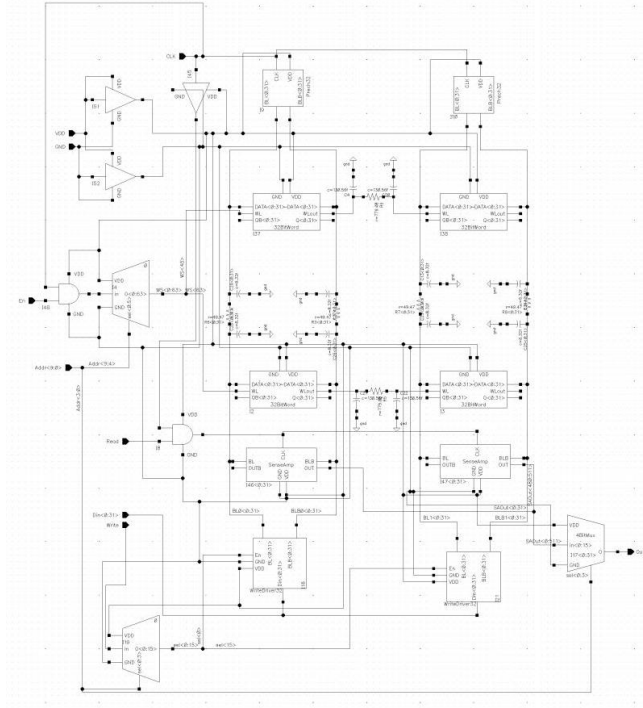

1.7 Full Model

Finally, we integrated all the previous parts together to generate a full model. This includes 32 blocks, adding up to 1Mb in total. The following sections assess the metrics of said model.

Figure 7. Full SRAM Hierarchy Schematic

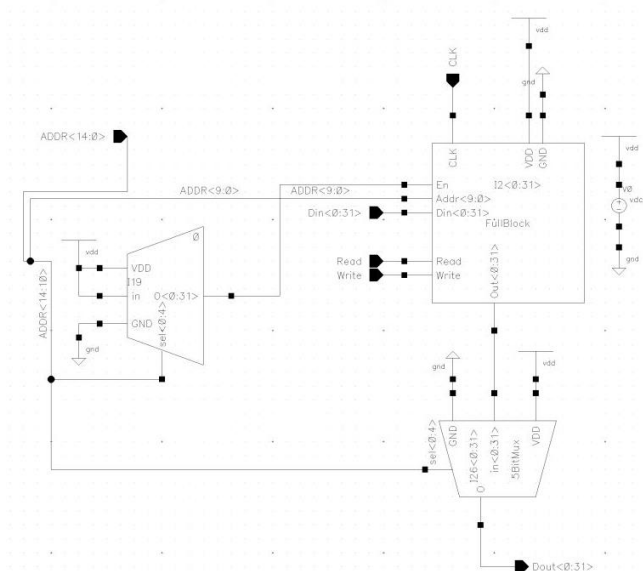

2. METRICS

2.1 Area

We found our bitcell area by adding up all the gate widths of all transistors in the model. This gave us the following figure:

Total Area: 27.49 mm

2.2 Delay

We were unable to calculate the delay, so we instead simulated it in a working block. Below show the propagation delays of all our read / write circuitry, respectively:

Figure 8. Read Propagation Delay Simulation


 


Figure 9. Write Propagation Delay Simulation

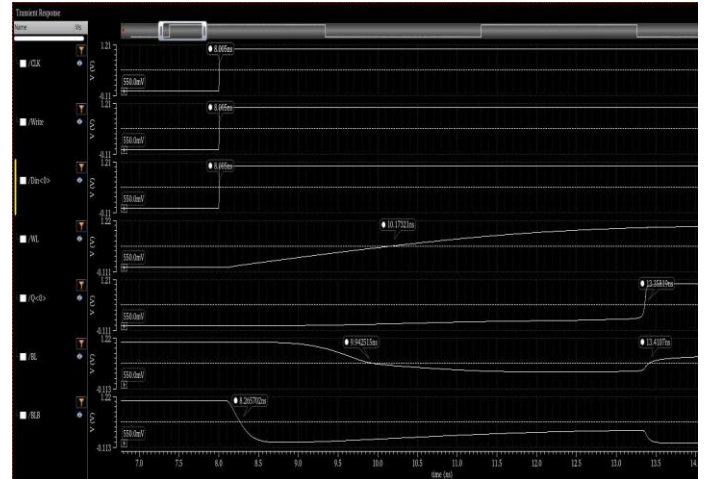

From these, we collected the following:

Read Delay: 0.865ns

Write Delay: 5.353ns

Total Delay: 5.353ns

Maximum Frequency: 186.811MHz

2.3 Energy

By reading the current and voltage draw from VDD for each block, we were able to establish values for idle, read and write power, and extrapolate to the entire model, as notated below:

Idle Power: $32 \cdot (1.1 \cdot 0.352) = 12.39\text{mW}$

Write Power: 27.0514mW

Write Energy: $27.0514\text{mW} \cdot 5.353\text{ns} = 144.5318\text{pJ} / \text{access}$

Read Power: 22.8734mW

Read Energy: $22.8734\text{mW} \cdot 5.353\text{ns} = 122.4413\text{pJ} / \text{access}$

Total Energy: $[5(122.4413\text{pJ}) + 1(144.5318\text{pJ})] / 6 = 124.2897\text{pJ} / \text{access}$

2.4 Summary

Metric	$2.816 \cdot 10^{-29} \text{ J}^2 \cdot \text{sec} \cdot \text{mm} \cdot \text{W}$
Total Area	27.49 mm
Read Energy	122.4413pJ
Write Energy	144.5318pJ
Total Energy	124.2897pJ
Read Delay	0.865ns
Write Delay	5.353ns
Total Delay	5.353ns
Idle Power	12.39mW

3. CONCLUSION

Looking at our final metric, we feel accomplished in that we were able to do what we set out to: we were able to develop a fast, low-power SRAM model that adheres to the previously laid out specifications. If one were to continue to pursue this architecture, it seems like decreasing write delay would go a long way to

bettering the metric. Namely, it may be worth looking into having 256 cells per row, as the main time-sink came from charging the wordlines to enable a write operation. There is also a large deal of optimization that may come from using a differing layout: we used FreePDK45 throughout, but if one were to design their own MOSFETs, there would be potential for large power savings, as well as better accuracy in simulation figures. As previously stated, we were able to simulate our model across different process variations, modeling the SNM, RNM and WNM plots in the TT, FF, SS, FS, and SF process corners, as well as with voltage variation ($V_{DD} = 1.1\text{V}$, $V_{DD} = 1.21\text{V}$, $V_{DD} = 0.99\text{V}$), and at temperatures of 0C, 27C and 50C.

4. ACKNOWLEDGMENTS

Our thanks to Professor Calhoun as well as Anjali Agrawal and Aki Takana for their guidance and feedback throughout the semester. Their support and dedication to their field inspired us time and time again to keep moving forward.

5. REFERENCES

- [1] B. Razavi, "The StrongARM Latch [A Circuit for All Seasons]," in IEEE Solid-State Circuits Magazine, vol. 7, no. 2, pp. 12-17, Spring 2015, doi: 10.1109/MSSC.2015.2418155.

6. APPENDIX

Model Area Calculations

Bitcell Area: $2 \cdot 150\text{nm} + 2 \cdot 90\text{nm} + 2 \cdot 150\text{nm}$

Total Bitcells Per block: $512 \cdot 64$

Total Precharge per block: $512 \cdot 2 \cdot 90\text{nm}$

Sense Amp Area: $11 \cdot 90\text{nm}$

Sense Amps Per Block: 512

Row Demux: $(16 \cdot 64 + 8) \cdot 90\text{nm}$

Column Demux: $(12 \cdot 16 + 8) \cdot 90\text{nm}$

Block Demux: $(14 \cdot 32 + 8) \cdot 90\text{nm}$

4 bit Mux: $(15 \cdot 16 \cdot 16 \cdot 90\text{nm})$

5 bit Mux: $(31 \cdot 32 \cdot 16 \cdot 90\text{nm})$

Total Area: 27.49 mm